


Dual Voltage Clipper Circuit

This circuit is a voltage clipper that will prevent the output signal from rising above or dropping below the forward voltage of the diode.

Components

- 2x 1N4148 small signal diodes
- 10 k Ω resistor

Schematic

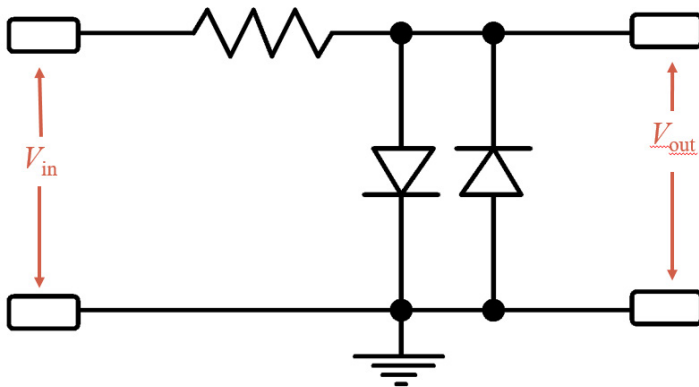

Circuit

