


Flyback Protection Circuit

This circuit uses a flyback diode to protect against potentially damaging flyback voltage spikes created by inductive components like the motor in an electric fan.

Components

- 5 VDC power source
- 5 VDC fan or motor
- 1N4148 small signal diodes
- Switch

Schematic

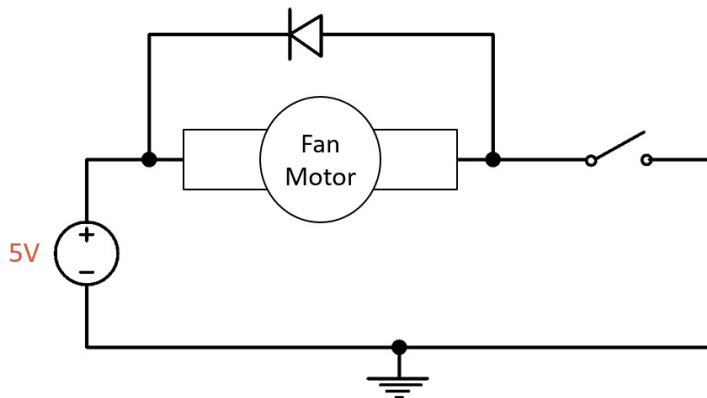

Circuit

