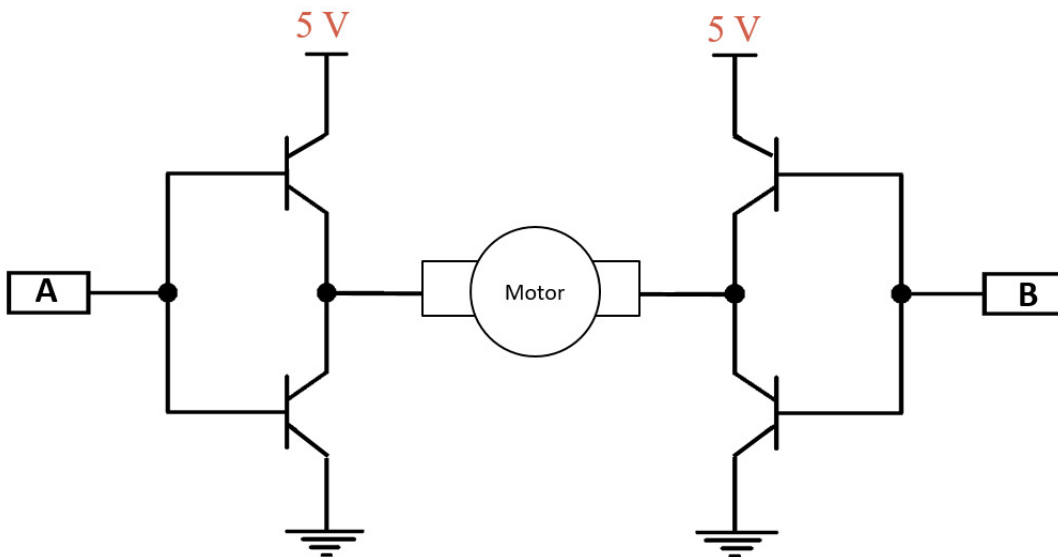


Control an A Motor

Challenge: Create an H-bridge circuit that can control a DC motor to make it spin in either direction.

Circuit Diagram



Goals

- Determine which transistors should be NPN.
- Determine which transistors should be PNP.
- Determine how each one should be oriented.

Bonus

- Determine where to place current limiting resistors in the H-bridge.

